

Date: 2012-11-02 (5 hours)

Allowed aids: none

Responsible Teacher: Mikael Bylund, tel: 060-148748, e-mail: mikael.bylund@miun.se

Number of tasks: 9

Number of pages: 3

Maximum points: 100 (50 points required to pass)

Instructions for submitted solutions:

- Rationale and justifications may not be so scarce that they become difficult to follow.
- The reasoning behind used equations should be explained.
- The calculations shall be sufficiently complete to show how the final result was obtained.
- Each task must be concluded with a clearly written answer.

1. **Convert the octal number 5263 into binary. Then convert the obtained binary number into hexadecimal. (8p)**
2. **Convert the decimal number -37 into an 8-bit binary number in two's complement form. (8p)**
3. **Minimize the following Boolean expression: $\overline{a+b} + a \cdot b + \overline{a \cdot b} + \overline{a} \cdot \overline{b}$ (10p)**
4. **Determine if the following equality is true: $\overline{c \cdot (\overline{a+b}) \cdot (a+b)} \cdot (b + \overline{bc} + abc) = ab + c$ (10p)**
5. **Minimize the function $f(x_3, x_2, x_1, x_0) = \sum(1,2,3,7,8,12) + d(0,5,10,15)$ by using a Karnaugh map. Write the function as a minimal sum-of-product (SP) expression. (10p)**
6. **Design a function that takes a 4-bit binary number $X = X(x_3, x_2, x_1, x_0)$ as input, calculates $|X - 7|$, and gives the result as a 4-bit binary number on the output ($| \cdot |$ indicates absolute value).
Give your answer as Boolean expressions for the output bits. (12p)**

7. Write a function in VHDL that takes a 5-bit input vector (4 bit data + 1 bit for odd parity), and then verifies if the parity bit matches the data or not (i.e. checks if the data has been correctly transmitted). (12p)
8. Draw the state transition graph for the VHDL code given in Appendix 1. Is this a Moore or a Mealy machine? Explain your reasoning. (14p)
9. Develop a circuit diagram for the state transition graph given below. Use Binary coding and T flip-flops for the state memory. (16p)

 


Figure 1

APPENDIX 1.

```
entity seq_design is
port(      a, clock, reset: in std_logic;
      x: out std_logic
);
end seq_design

architecture FSM of seq_design is
    type state_type is (S0, S1, S2, S3);
    signal next_state, current_state: state_type;

    process(clock, reset)
    begin
        if (reset='1') then
            current_state <= S0;

        else
            case current_state is

                when S0 => if a='0' then
                            next_state <= S1;
                            x <= 1;
                        elsif a='1' then
                            next_state <= S2;
                            x <= 0;
                        end if;

                when S1 => if a='0' then
                            next_state <= S1;
                            x <= 1;
                        elsif a='1' then
                            next_state <= S2;
                            x <= 0;
                        end if;

                when S2 => if a='0' then
                            next_state <= S2;
                            x <= 1;
                        elsif a='1' then
                            next_state <= S3;
                            x <= 0;
                        end if;

                when S3 => if a='0' then
                            next_state <= S0;
                            x <= 0;
                        elsif a='1' then
                            next_state <= S3;
                            x <= 1;
                        end if;

            end case;
        endif;

        current_state <= next_state;

    end process;
end FSM;
```