



1)

HEX	BIN
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
A	1010
B	1011
C	1100
D	1101
E	1110
F	1111

$$DB3_{16} = \underline{1101\ 1011\ 0011}_2$$

to convert from binary to octal a easy way its  
to group the binary number into 3 bits group.

$$110\ 110\ 110\ 011_2 = \underline{6663}_8$$

KOD: S61

BLAD NR: 02



Mittuniversitetet  
MID SWEDEN UNIVERSITY

		quotient	remainder	
2)	$35_{10}$ in binary is:	$35/2$	17	1 Least significant bit
		$17/2$	8	1
		$8/2$	4	0
		$4/2$	2	0
		$2/2$	1	0
		$1/2$	0	1 Most significant bit

10 0011

In 8-bit binary: 0010 0011<sub>2</sub>

$-35_{10}$  : Invert: 0010 0011<sub>2</sub>  
1101 1100<sub>2</sub>

add +1 to the inverted binary number

1101 1100  
+ 1

Answer: 1101 1101<sub>2</sub>  $\Rightarrow -35_{10}$



$$3) (x + y + z)(x + y + \bar{z})$$

$$= \underbrace{xx}_{=x} + xy + x\bar{z} + yx + \underbrace{yy}_{=y} + y\bar{z} + zx + zy + \underbrace{z\bar{z}}_{=0}$$

$$= x + xy + x\bar{z} + yx + y + y\bar{z} + zx + zy =$$

$$= x(1 + \underbrace{y + \bar{z}}_{=1}) + y(1 + \underbrace{\bar{z} + z}_{=1})$$

$$= x(\underbrace{1 + 1}_{=1}) + y(\underbrace{1 + 1}_{=1})$$

$$= \underline{x + y}$$



$$4) \overline{a + bc} \cdot \overline{a(b+c)} = 0$$

$$\text{Left Hand side (LHS)} = \overline{a + \overline{bc}} \cdot \overline{a(b+c)} \quad \text{by De Morgan's law (1)}$$

$$= \overline{(a + \overline{b + c})} \cdot \overline{(\overline{ab} + \overline{ac})} \quad \text{by De Morgan's law (2)}$$

$$= (\overline{a} + \overline{\overline{b}} + \overline{\overline{c}}) (\overline{\overline{ab}} + \overline{\overline{ac}}) \quad \text{by De Morgan's law (1)}$$

$$= (\overline{a} + b + c) (\overline{a} + \overline{b}) (\overline{a} + \overline{c})$$

$$= \overline{a} b c (a + \overline{b}) (a + \overline{c})$$

$$= \overline{a} b c (\underbrace{aa}_{=a} + a\overline{c} + \overline{b}a + \overline{b}\overline{c})$$

$$= \underbrace{a\overline{a}}_{=0} b c + \underbrace{a\overline{c}b\overline{c}}_{=0} + \underbrace{\overline{a}a}_{=0} \underbrace{b\overline{b}}_{=0} c + \underbrace{\overline{a}b\overline{b}c}_{=0} + \underbrace{\overline{a}b\overline{b}c\overline{c}}_{=0}$$

$$= 0 = \text{Right Hand side (RHS)}$$

QED

De Morgan's law:

$$\bullet \overline{X} + \overline{Y} = \overline{XY} \quad (1)$$

$$\bullet \overline{X} \cdot \overline{Y} = \overline{X+Y} \quad (2)$$

KOD: S61

BLAD NR: 05



Mittuniversitetet  
MID SWEDEN UNIVERSITY

5)

Row	$x_3$	$x_2$	$x_1$	$x_0$	output
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	-
5	0	1	0	1	-
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	-
10	1	0	1	0	-
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	-

Karnaugh - map

$x_1 x_0$	$x_3 x_2$	00	01	11	10
00	0	1	0	0	0
01	-	-	1	1	-
11	0	1	-	0	0
10	0	-	0	-	-

$\overline{x}_3 x_2$  (grouping the first two rows)  
 $\overline{x}_1 x_0$  (grouping the first two columns)


Answer :  $f(x_3, x_2, x_1, x_0) = \overline{x}_3 x_2 + \overline{x}_1 x_0$




6)

table:

INPUT			OUTPUT	
$x_2$	$x_1$	$x_0$	$z_1$	$z_0$
0	0	0	1	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	0	0

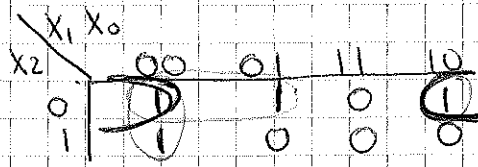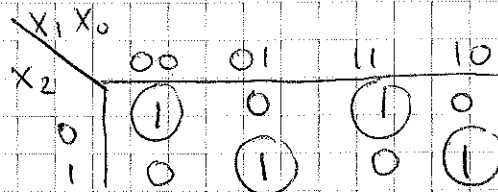for  $z_1$ :

$$z_1 = \bar{x}_1 \bar{x}_0 + \bar{x}_2 \bar{x}_1 + \bar{x}_2 \bar{x}_0$$

for  $z_0$ :

$$z_0 = \bar{x}_2 \bar{x}_1 \bar{x}_0 + x_2 \bar{x}_1 x_0 + \bar{x}_2 x_1 x_0 + x_2 x_1 \bar{x}_0$$



```

7) entity oddparity is
    Port ( in1 : in std_logic_vector (3 downto 0);
          parity : in std_logic;
          out1 : out std_logic_vector (4 downto 0));
end oddparity;

```

architecture rtl of oddparity is

begin

```

    Process ( in1, parity)

```

```

        Variable op : std_logic_vector (3 downto 0);

```

```

    begin

```

```

        op := in1;

```

```

        Case op is

```

```

            when "0000" => parity <= '1'; out1 <= "10000";
            when "0001" => parity <= '0'; out1 <= "00001";
            when "0010" => parity <= '0'; out1 <= "00010";
            when "0011" => parity <= '1'; out1 <= "10011";
            when "0100" => parity <= '0'; out1 <= "00100";
            when "0101" => parity <= '1'; out1 <= "10101";
            when "0110" => parity <= '1'; out1 <= "10110";
            when "0111" => parity <= '0'; out1 <= "00111";
            when "1000" => parity <= '0'; out1 <= "01000";
            when "1001" => parity <= '1'; out1 <= "11001";
            when "1010" => parity <= '1'; out1 <= "11010";
            when "1011" => parity <= '0'; out1 <= "01011";
            when "1100" => parity <= '1'; out1 <= "11100";
            when "1101" => parity <= '0'; out1 <= "01101";
            when "1110" => parity <= '0'; out1 <= "01110";
            when "1111" => parity <= '1'; out1 <= "11111";
            when others => parity <= '0'; out1 <= "00000";

```

```

        end case;

```

```


    end process;

```

```

end rtl;

```

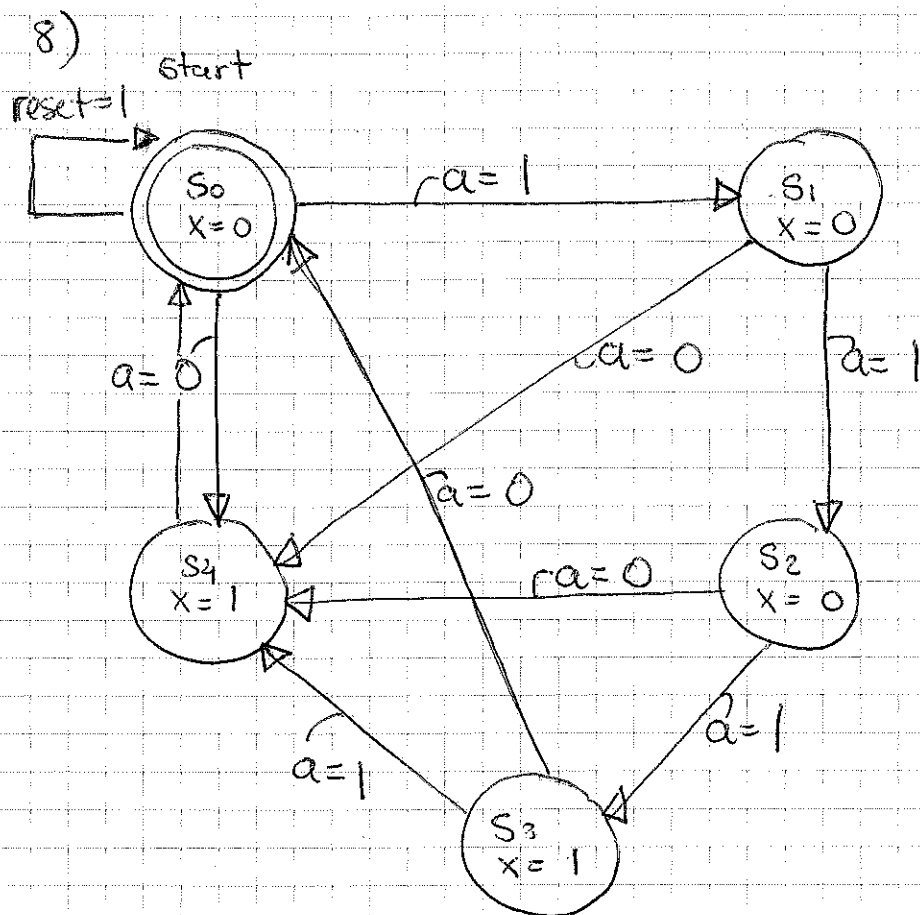





9)

State table:

S	X		Z
	0	1	
A	B	C	0
B	C	D	0
C	B	D	1
D	C	A	0

 $\Rightarrow$ binary coding:

State(S)	Binary(Q)
A	00
B	01
C	10
D	11

transition table:

Q	X		Z
	0	1	
00	01	10	0
01	10	11	0
10	01	11	1
11	10	00	0
$q_1, q_0$		$Q^+$	

D flip-flop:  $q^+ = D$ 

q	$q^+$	D
0	0	0
0	1	1
1	0	0
1	1	1

 $\Rightarrow$ Excitation table:

Q	X		Z
	0	1	
00	01	10	0
01	10	11	0
10	01	11	1
11	10	00	0

 $Q = \{q_1, q_0\}$  $D = \{d_1, d_0\}$ •  $\delta$  function:

X \ $q_1, q_0$	00	01	11	10
0	0 <sub>0</sub>	1 <sub>1</sub>	1 <sub>3</sub>	0 <sub>2</sub>
1	1 <sub>4</sub>	1 <sub>5</sub>	0 <sub>7</sub>	1 <sub>6</sub>

X \ $q_1, q_0$	00	01	11	10
0	1 <sub>0</sub>	0 <sub>1</sub>	0 <sub>3</sub>	1 <sub>2</sub>
1	0 <sub>4</sub>	1 <sub>5</sub>	0 <sub>7</sub>	1 <sub>6</sub>

$$d_1 = \bar{q}_1 \bar{q}_0 + \bar{X} q_0 + X \bar{q}_0$$

$$d_0 = \bar{X} \bar{q}_0 + q_1 \bar{q}_0 + X \bar{q}_1 q_0$$

•  $\Lambda$  function:

$q_1, q_0$	00	01	11	10
	0	0	0	1

$$Z = \bar{q}_1 \bar{q}_0$$

9) Circuit Diagram :