

Date: 2012-05-29 (5 hours)

Allowed aids: none

Responsible Teacher: Mikael Bylund, tel: 073-7272926, e-mail: mikael.bylund@miun.se

Number of tasks: 9

Number of pages: 3

Maximum points: 100 (50 points required to pass)

Instructions for submitted solutions:

- Rationale and justifications may not be so scarce that they become difficult to follow.
- The reasoning behind used equations should be explained.
- The calculations shall be sufficiently complete to show how the final result was obtained.
- Each task must be concluded with a clearly written answer.

1. **Convert the hexadecimal number DB3 into binary. Then convert the obtained binary number into octal. (8p)**
2. **Convert the decimal number -35 into an 8-bit binary number in two's complement form. (8p)**
3. **Minimize the following Boolean expression: $(x + y + z)(x + y + \bar{z})$ (10p)**
4. **Determine if the following equality is true: $\overline{a + b \cdot c} \cdot \overline{a \cdot (b + c)} = 0$ (10p)**
5. **Minimize the function $f(x_3, x_2, x_1, x_0) = \sum(1, 6, 7, 13) + d(4, 5, 9, 10, 15)$ by using a Karnaugh map. Write the function as a minimal sum-of-product (SP) expression. (10p)**
6. **Design a function that counts how many of the bits in the input-vector $X = (x_2, x_1, x_0)$ that are 0. The result should be given as a binary number on the output $Z = (z_1, z_0)$.
Give your answer as a Boolean expression. (12p)**

7. Write a function in VHDL that takes a 4-bit vector as input, determines the parity bit required for odd parity, and gives a 5-bit output that contains the parity bit and the original 4-bit vector. (12p)
8. Draw the state transition graph for the VHDL code given in Appendix 1. (14p)
9. Develop the circuit diagram for the state transition graph given below. Use D flip-flops and binary coding for the state memory. (16p)

 


Figure 1

APPENDIX 1.

```
entity seq_design is
port(      a, clock, reset: in std_logic;
      x: out std_logic
);
end seq_design

architecture FSM of seq_design is
    type state_type is (S0, S1, S2, S3, S4);
    signal next_state, current_state: state_type;

begin
    process(clock, reset)
    begin
        if (reset='1') then
            current_state <= S0;
        elsif (clock'event and clock='1') then
            current_state <= next_state;
        end if;
    end process;

    process(current_state, a)
    begin
        case current_state is
            when S0 => x <= '0';
                        if a='0' then
                            next_state <= S4;
                        elsif a='1' then
                            next_state <= S1;
                        end if;
            when S1 => x <= '0';
                        if a='0' then
                            next_state <= S4;
                        elsif a='1' then
                            next_state <= S2;
                        end if;
            when S2 => x <= '0';
                        if a='0' then
                            next_state <= S4;
                        elsif a='1' then
                            next_state <= S3;
                        end if;
            when S3 => x <= '1';
                        if a='0' then
                            next_state <= S0;
                        elsif a='1' then
                            next_state <= S4;
                        end if;
            when S4 => x <= '1';
                        next_state <= S0;

        end case;
    end process;
end FSM;
```