

Exam – ET061G – 9 Juni 2021

Digitalteknik med VHDL

Time	4 hours
Support material	none
No. of questions	6
No. of pages	6
No. of points	50 (25 for passed)

- Please hand in one task per page.
- Rationale may not be so scarce that they become difficult to follow.
- Reasoning behind equations should be explained.
- Calculations shall be sufficiently complete to show how the result was obtained.
- Each task must be concluded with a clearly written answer.
- The exam must be solved individually.

David Krapohl, tel: 010-142 8755, e-post: david.krapohl@miun.se

Tasks

Exercise 1.

- a) Convert the following octal number to hexadecimal, decimal using binary numbers notation: 3 P.

$$71.72_8$$

- b) Use the shift operation to calculate the binary result using 8-bit registers: 2 P.

$$01101010_2 \div 16_{10}$$

- c) Calculate $33 - 37$ using 8 bit registers. 2 P.

Exercise 2.

- a) Determine if the following equality is true: 4 P.

$$\overline{xy + xy \cdot \overline{x} \cdot \overline{y}} = (\overline{xy} + \overline{xy}) \cdot 1$$


- b) Minimise the following Boolean equation: 4 P.

$$abc + ab + (\overline{ac} \cdot a + \overline{ac} \cdot a)$$

- c) Minimise the function $f(abcd) = \sum(2, 5, 10, 13) + d(7, 13)$ to product of sums-form with the help of a Karnaugh-map. Draw a gate level diagram for the minimised expression. 5 P.

Exercise 3.

Create the Boolean expressions that describe the behaviour of the state graph below. 6 P.
Use binary code and T-flipflops. The characteristic equation is $Q^+ = \bar{T}Q + T\bar{Q}$ (hint: rewrite to table).

 


Exercise 4.

a) Draw a gate level diagram for the equation below and complete the waveform output for X.

$$X = \overline{AB} + A\overline{B} + C\overline{D} + DE + \overline{B}C \quad (1)$$


2 P.

 

2 P.

b) Decide on the type of device and complete the timing diagram for Q. You can draw in the image and include it into your submission.

4 P.

 

Exercise 5.

Below is a state machine in VHDL code. What kind of state machine is it? What does it do? Draw the state diagram with all inputs and states!

9 P.

```

1 library ieee;
2 use ieee. std_logic_1164.all;
3
4 entity seqdata is
5     port (clk: in std_logic; -- klocka
6           clr: in std_logic; -- starta om
7           din: std_logic;    -- sekvens input

```

```

8         z: out std_logic); -- output
9 end seqdata;
10
11 architecture seqdata of seqdata is
12 type state_type is (s0, s1, s2, s3, s4);
13 signal present_state, next_state: state_type;
14
15 begin
16
17 sres: process(clk, clr) -- reset och forandring av tillstand
18     begin
19         if clr = '1' then
20             present_state <= s0;
21         elsif clk'event and clk = '1' then
22             present_state <= next_state;
23         end if;
24     end process;
25
26 state: process (present_state, din) -- logik for tillstand
27     begin
28         case present_state is
29             when s0 =>
30                 if din = '0' then
31                     next_state <= s1;
32                 else
33                     next_state <= s0;
34             when s1 =>
35                 if din = '1' then
36                     next_state <= s2;
37                 else
38                     next_state <= s1;
39             when s2 =>
40                 if din = '1' then
41                     next_state <= s3;
42                 else
43                     next_state <= s1;
44             when s3 =>
45                 if din = '0' then
46                     next_state <= s4;
47                 else
48                     next_state <= s2;
49             when s4 =>
50                 if din = '1' then
51                     next_state <= s2;
52                 else
53                     next_state <= s1;

```


```

54     when others =>
55         null;
56     end case;
57 end process;
58
59 outp: process (present_state) -- output
60     z <= '1';
61     if present_state = 's4' then
62         z <= '0';
63     end process;
64
65 end seqdata;


```

Exercise 6.

 - a) Draw or describe the signal behaviour for A, B and C with respect to delta delay when the input signal switches from 0 to 1. 4 P.



 - b) Calculate the maximum gate delay path for the following gate level circuit with the given delays. 3 P.



Gates Delay	
inverter	0.1ns
nand	0.4ns
and	0.9ns
or	0.3ns