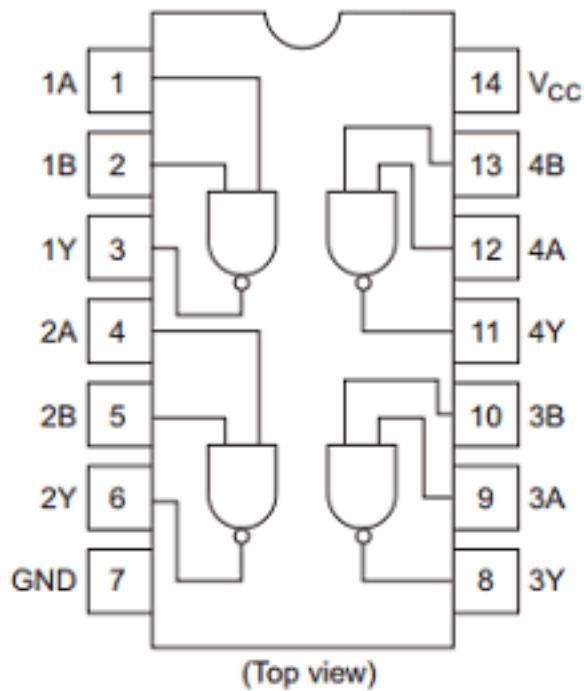


Johannes Joujo

Task 1



[Länk](#)

Port 1 and 2 are 1A and 1B into a nand gate that gives the result to the 1Y.

Port 4 and 5 are 2A and 2B into a nand gate that gives the result to 2Y.

Number 7 is ground.

Number 14 is the common collector voltage.

In the same was as above 4B and 4A goes into a nand gate and give the result through port 11 which is 4Y.

Port 10 and 9 goes into a nand gate that gives the result to port 8.

Task 2

K-map


	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	1	1	0	0
10	1	1	0	0

C

T table


A	B	C	D	W
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0

$\bar{Z} + \bar{A}(\bar{B} + ABD)$ från K-map
 $\bar{Z} + \bar{A}\bar{B} + ABD$ Absorption law
 $\bar{Z} + \bar{B}(A\bar{B} + \bar{A})$ Dist. law
 $\bar{Z} + \bar{B}(B + \bar{A})$ Abs. law
 $\bar{Z} + \bar{B}B + \bar{B}\bar{A}$ Dist. law




Vi behöver fler hos oss som du.
Och du. Och du. Läs mer på peab.se

Task 3

 

Task 4

 

I was thinking that B and D' would go in to the first and gate with two 1 because the result will still be dependent on the value of B and D'. Same with A' and D'. The outputs go into an nor gate with C', because it's a nor gate I use it again to switch the values back to what they are supposed to be.

3 report

I searched 74HC00 and copied a picture of the circuit, I also searched what each port does.

In task 2 I used my knowledge and drew a k-map with a truth table. I paired the ones and got a expression from the k-map I later simplified it with the laws.

In task 3 I followed the simplified version of that expression and used gates to visualize it, I used the truth table to control if it was correct and it gave the same answers on the output.

In task 4 I found an AND and an XOR 74HC00 series that I could use.

