

*Exam – ET061G – 22 Augusti 2019*

## **Digitalteknik med VHDL**

Time	5 hours
Support material	none
No. of questions	6
No. of pages	7
No. of points	50 (25 for passed)

- Please hand in one task per page.
- Rationale may not be so scarce that they become difficult to follow.
- Reasoning behind equations should be explained.
- Calculations shall be sufficiently complete to show how the result was obtained.
- Each task must be concluded with a clearly written answer.

David Krapohl, tel: 010-142 8755, e-post: david.krapohl@miun.se

## Tasks

### Exercise 1.

- a) Convert the following decimal number to hexadecimal, octal and binary notation: 3 P.

$$15.25_{10}$$

- b) Use the left-shift operation to calculate the binary result using 8-bit registers: 2 P.

$$111011_2 \times 8_{10}$$

- c) Calculate two's complement of  $-39$  using 8 bit registers. 2 P.

### Solution 1.

- a)

$$\begin{array}{r} \text{binary: } 001111.01_2 \\ \hline \begin{array}{ccc} \underline{001} & \underline{111} & \underline{.010} \\ 1 & 7 & 2 \end{array} \\ \hline \begin{array}{ccc} \underline{1111} & \underline{.0100} \\ F & 4 \end{array} \end{array}$$

$$\text{octal: } 17.2_8$$

$$\text{hex: } F.4_{16}$$

- b) vänsterskift 3x

$$\begin{array}{l} 111011 \ll 3 \\ \Rightarrow [1]11011000_2 \end{array}$$

- c)  $-39$  in two's complement with 8 bit registers.

$$\begin{array}{r} 0010\ 0111 \\ \Rightarrow 1101\ 1000 \\ +\ 0000\ 0001 \\ =\ 1101\ 1001 \end{array}$$

### Exercise 2.

a) Determine if the following equality is true:

4 P.

$$(a + \bar{b})c = (a\bar{b}c) + (\bar{a}\bar{b})c$$

b) Minimise the following Boolean equation:

4 P.

$$\bar{a} \cdot \bar{c} \cdot \bar{d} + \overline{(a \cdot d)}$$

c) Minimise the function  $f(abcd) = \sum(0, 5, 6, 7, 8, 9, 13, 14, 15) + d(2, 4, 10, 12)$  with the help of a Karnaugh-map. Draw a gate level diagram for the minimised expression.

5 P.

### Solution 2.

a) yes, they are the same.

$$\begin{aligned} &= a\bar{b}c + (\bar{a} + \bar{b})c \\ &= a\bar{b}c + ac + \bar{b}c \\ &= (a\bar{b} + a + \bar{b})c \\ &= (a(\bar{b} + 1) + \bar{b})c \\ &= (a + \bar{b})c \end{aligned}$$

b) Fastest solution:

$$\begin{aligned} &= \bar{a} \cdot \bar{c} \cdot \bar{d} + \overline{a \cdot d} \\ &= \bar{a} \cdot \bar{c} \cdot \bar{d} + \bar{a} + \bar{d} \\ &= \bar{a}(\bar{c} \cdot \bar{d} + 1) + \bar{d} \\ &= \bar{a} + \bar{d} \end{aligned}$$


		<i>cd</i>			
		00	01	11	10
<i>ab</i>	00	1	0	0	—
	01	—	1	1	1
	11	—	1	1	1
	10	1	1	0	—

c)

$$f = \bar{d} + b + a\bar{c}$$
 
### Exercise 3.

Develop Boolean expressions that model the behaviour of the state machine below. 6 P.  
Use binary coding and D-flipflops.



### Solution 3.

State table

	0	1
A	A B 1	
B	A C 1	
C	B D 0	
D	B A 0	

Transition table

	0	1
00	00 01 1	
01	00 10 1	
10	01 11 0	
11	01 00 0	

Excitation table

	0	1
00	00 01 1	
01	00 10 1	
10	01 11 0	
11	01 00 0	

$q_1q_0$

	00	01	11	10
0	0	0	0	0
1	0	1	0	1

$$d_0 = E\bar{q}_1q_0 + Eq_1\bar{q}_0$$

$q_1q_0$

	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$d_1 = \bar{E}q_1 + q_1\bar{q}_0 + E\bar{q}_0$$


$$z = \bar{q}_1$$

**Exercise 4.**

Draw a gate level diagram for the equation below and complete the waveform output for X.

$$X = AB + \overline{A}B + C\overline{D} + D\overline{E} + \overline{B}C \quad (1)$$

4 P.

 

4 P.

**Solution 4.****Exercise 5.**

Write the truth table and draw the gate level diagram for a full adder. Complete the VHDL code below to achieve the same functionality. XOR can be used. 9 P.

```

1      library IEEE;
2      use IEEE.STD_LOGIC_1164.all;
3
4      entity full_adder is
5          Port ( a : in STD_LOGIC;
6                b : in STD_LOGIC;
7                Cin : in STD_LOGIC;
8                sum : out STD_LOGIC;
9                Cout : out STD_LOGIC);
10     end full_adder;
11
12     architecture behaviour of full_adder is
13     begin
14         -----
15         -- <<<write your code here>>>
16         -----
17     end behaviour;

```

### Solution 5.

Different solutions possible

```


1
2
3 -----
4     sum <= a xor b xor Cin;
5     Cout <= ((a xor b) and Cin) or (a and b);

```

### Exercise 6.


- a) Draw or describe the signal behaviour for A, B and C with respect to delta delay when the input signal switches from 1 to 0.

4 P.

 


- b) Calculate the maximum gate delay path for the following gate level circuit with the given delays.

3 P.

 

Gates Delay	
inverter	0.1ns
nand	0.4ns
and	0.9ns
or	0.3ns

**Solution 6.**

 

a)  $T \quad T+\Delta \quad T+2\Delta \quad T+3\Delta \quad T+4\Delta$

b) Gate delays:

$$0.3ns + 0.4ns + 0.4ns = \underline{1.1ns}$$