

# Mid Sweden University

*Exam – ET061G– March 16 2015*

## Digital Electronics with VHDL

Time: five hours

Allowed aids: None

Number of tasks: 9

Number of pages: 5

Maximum points: 100 (50 are required to pass)


David Krapohl, tel: 060-148755, email: david.krapohl@miun.se

Instructions for submitted solutions:

- Rationale and justifications may not be so scarce that they become difficult to follow.
- The reasoning behind used equations should be explained.
- The calculations shall be sufficiently complete to show how the final result was obtained.
- Each task must be concluded with a clearly written answer.

## Tasks

 - Exercise 1.** 8 P.  
Covert the following binary number to hexadecimal and ocatal form:  
11001001001
- Exercise 2.** 8 P.  
Convert the decimal number -51 to an 8-bit binary number in two's complement form.
- Exercise 3.** 10 P.  
Minimize the following Boolean expression:  $a \cdot \bar{b} + \overline{a \cdot \bar{c} \cdot d} + a \cdot c + d \cdot c$
- Exercise 4.** 10 P.  
Determine if the following equality is true:  $x \cdot \bar{y} \cdot z + \bar{x} \cdot \bar{z} = (\bar{x} + \bar{y})(\bar{x} + z)(x + \bar{z})$
- Exercise 5.** 10 P.  
Minimize the function  $f(a, b, c, d) = \sum(0, 5, 7, 10, 13, 15) + d(2, 8)$  by using a Karnaugh-diagram. Write the result as a minimal Sum-of-Product (SoP) expression.
- Exercise 6.** 12 P.  
Design a function that takes the binary numbers  $X = (x_1, x_0)$  and  $Y = (y_1, y_0)$  as inputs and compares the numbers. The output  $Z = (z_2, z_1, z_0)$  should show if X is smaller ( $z_2 = 1$ ), equal to ( $z_1 = 1$ ) or larger than ( $z_0 = 1$ ) Y. Give your answer as Boolean expressions for the output bits.
- Exercise 7.** 12 P.  
Write VHDL-code for the function described in task 6.
- Exercise 8.** 14 P.  
Draw the state transition graph for the VHDL code given in Appendix 1. Is this a Moore or a Mealy machine? Explain your reasoning.
- Exercise 9.** 16 P.  
Develop a circuit diagram for the state transition graph shown below. Use gray code and T-flip-flops for the state memory.



## Appendix

```
\begin{verbatim}
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity seqdet is
    port (clk: in std_logic;
          clr: in std_logic;
          din: in std_logic;
          dout: out std_logic);
end seqdet;

architecture seqdet of seqdet is

    type state_type is (s0,s1,s2,s3,s4);
    signal present_state, next_state: state_type;

begin
    sreg: process(clk, clr)
    begin
        if clr = '1' then
            present_state <= '0';
        elsif clk'event and clk = '1' then
            present_state <= next_state;
        end if;
    end process;

    C1: process(present_state, din)
    begin
        case present_state is
            when s0 =>
                if din = '1' then
                    next_state <= s1
                else
                    next_state <= s0;
                end if;
            when s1 =>
                if din = '1' then
                    next_state <= s2
                else
                    next_state <= s0;
                end if;
        end case;
    end process;
end seqdet;
```

```

        when s2 =>
            if din = '1' then
                next_state <= s3
            else
                next_state <= s2;
            end if;
        when s3 =>
            if din = '1' then
                next_state <= s1
            else
                next_state <= s0;
            end if;
        when others =>
            null;
    end case;
end process;

seq2: process(clk, clr)
begin
    if clr = '1' then
        dout <= '0';
    elsif clk'event and clk='1' then
        if present_state = s3 and din = '1' then
            dout <= '1';
        else
            dout <= '0';
        end if;
    end if;
end process;
end seqdet;
\end{verbatim}

```